

Objective:

To design, simulate, synthesize and characterize following types of adders by creating Verilog models (of indicated types) that use only logical operators (and not any arithmetic operators):

- (1) 16-bit, 32-bit and 64-bit Unsigned Ripple Carry Adders that can also detect and signal arithmetic overflow caused by addition (behavioral Verilog module)
- (2) 16-bit, 32-bit and 64-bit Signed Ripple Carry Adders that can also detect and signal arithmetic overflow caused by addition (behavioral Verilog module)
- (3) A structural Verilog module for 32-bit Signed Redundant Carry Adder by defining and instantiating a behavioral module for 8-bit ripple carry adder, 8:1 multiplexor and 2:1 multiplexor. The adder should be able to detect and signal whenever the result of addition is zero
- (4) Study the behavioral Verilog code for a 64-bit Hierarchical Carry Look-Ahead Adder being provided to you. Check out this code for its logical correctness and syntactical correctness. Make corrections in the code as necessary and document the same.
- (5) Verify all the above designs through simulations. Synthesize all the above designs and tabulate your synthesis results: LUT count, delay and power